

MASSACHUSETTS INSTITUTE OF TECHNOLOGY

Department of Electrical Engineering

6.331 Advanced Circuit Techniques

Spring Term 2002
Problem Set 4

Issued : March 8, 2002
Due : Friday, March 15, 2002

Problem 1 The flyback converter shown in Figure 4.1 is operating in steady state with a constant frequency PWM-type switch drive at a switching frequency of 100kHz.

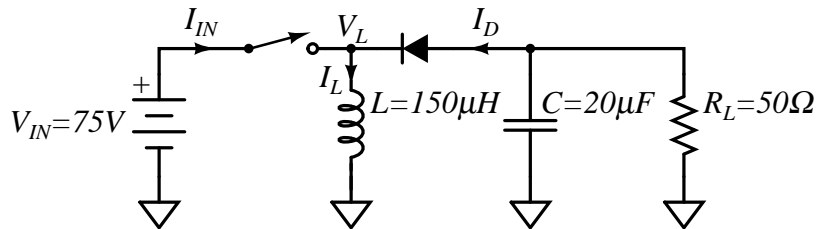


Figure 4.1: Flyback Converter

- A. Determine the relationship between the output voltage V_O , the input voltage V_I , and the duty cycle (D) of the switch drive. Explain why this topology is sometimes called a “buck-boost” or “up-down” converter.
- B. Assume that the duty cycle of the switch drive is $D = 0.4$. Determine the average value of i_{in} , the average value of v_{out} , and the peak-to-peak magnitude of the output voltage ripple. Sketch i_L and v_L for a switching cycle.
- C. Determine the transfer function which relates the incremental changes in output voltage to a small perturbation in D . Comment on the nature of this transfer function.
- D. Assume the on resistance of the switch is $R_{on} = 1\Omega$, and the forward voltage drop of the diode is $0.35V + 0.1\Omega i_D$. Estimate the power dissipation in the switch and the diode.

Problem 2 This problem examines the switching performance of a common base amplifier. The transistor parameters are $\beta_F = 100$, $\beta_R = 5$, $\tau_F = 0.5$ ns, $\tau_R = 1$ ns, and $\tau_S = 7.55$ ns. Ignore the effects of the space charge layers. The transistor is connected as shown in Figure 4.5.

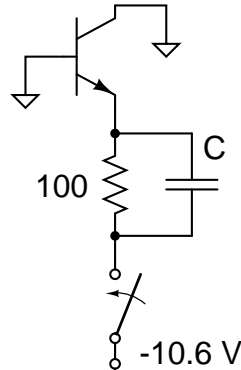


Figure 4.5: Switched-emitter common base amplifier

- A. Assume that $C = 0$ and $q_F = q_R = 0$ for $t < 0$. The switch is closed at time $t = 0$. Determine equations that describe the growth of q_F and i_C as functions of time.
- B. The test described above is repeated with capacitor C included. What value of C minimizes the time required for the transistor to reach steady-state values of q_F and i_C ?

Now suppose the circuit is changed to Figure 4.6 (you may assume that V_{CEsat} for the transistor is zero).

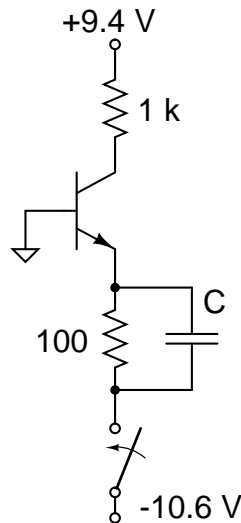


Figure 4.6: Switched-emitter common base amplifier

- C.** Again assume $C = 0$ and $q_F = q_R = 0$ for $t < 0$ and that the switch is closed at time $t = 0$. How long does the transistor remain in the forward-active region?
- D.** The switch is kept closed until the transistor reaches steady state in saturation. What are the values of q_F , q_R , q_{B0} , and q_S in the steady state? (Recall that q_{B0} is the base charge required to get to the edge of saturation.)
- E.** The test described in part C is repeated with capacitor C included. What value of C minimizes the time required to reach steady-state saturation?
- F.** Once steady-state saturation has been reached, the switch is opened. What is the value of i_B immediately after the switch is opened?
- G.** How long after the switch is opened does the transistor remain in saturation?
- H.** Sketch the general form of the base charge distribution shortly after the switch is opened (part F) and at the instant the transistor enters the forward active region (following the time determined in part G).